

# ALU Module Explained

**ALU** stands for **Arithmetic Logic Unit**.

It is the primary building block in any CPU for doing calculations—addition, subtraction, and various logic operations such as AND and OR.

Name	Dir.	Width	Description
a	input	32-bit	First operand
b	input	32-bit	Second operand
aluop	input	3-bit	Selects the operation to perform
y	output	32-bit	Result of the selected operation
zero	output	1-bit	True if result <code>y</code> is zero ( <code>y == 0</code> )

## Operation Selection

The `aluop` input chooses which calculation or logic operation the ALU should perform on inputs `a` and `b`:

aluop	Operation	Meaning
000	<code>y = a + b</code>	ADD
001	<code>y = a - b</code>	SUB
010	<code>y = a &amp; b</code>	AND (bitwise AND)
011	<code>y = a   b</code>	OR (bitwise OR)
other	<code>y = 0xDEAD_BEEF</code>	Default/error case

1. **Combinational Logic**

The result **y** is computed continuously based on the current inputs—no waiting for a clock; it's combinational.

2. **Zero Flag**

The **zero** output is set to **1** (true) if the result **y** equals zero. This is commonly used for branch decisions (**beq**, **bne**, etc.).

## Where does the ALU fit in the CPU?

- **EXE Stage:**

The ALU is the main component in the Execute (EXE) pipeline stage. It receives operands (numbers to operate on) and control signals (which operation to perform) from previous pipeline stages.

- **Arithmetic & Logic:**

All arithmetic (**add**, **sub**) and logical (**and**, **or**) operations in the CPU are performed here.

- **Branch Decisions:**

The **zero** output helps the CPU quickly check if two values are equal (used by branch instructions).